


### Part I: Multiple Choice

- B 1. Decimal number 46 in excess 3 code = \_\_\_\_\_.
- A. 1000 1001                      C. 0111 1111  
B. 0111 1001                      D. 1000 1111

2. For the gate in the given be

figure the output will

- A. 0  
B. 1  
C. A  
D.  $\bar{A}$

 

3. An AND gate with schematic "bubbles" on its inputs performs the same function as a(n) \_\_\_\_\_ gate.
- A. NOT                      B. OR                      C. NOR                      D. NAND

4. Full adder circuit can be implemented by
- A. Multiplexers  
B. Half adders  
C. AND or OR gates  
D. Decoders


- 13 5. A device which converts BCD to seven segments is called \_\_\_\_\_
- A. Encoder      B. Decoder      C. Multiplexer      D. Multiplexer

- C 6. Which one of the following can be used as parallel to series converter?
- A. Decoder
  - B. Digital counter
  - C. Multiplexer
  - D. DeMultiplexer

- A 7. As the number of flip flops are increased, the total propagation delay of
- A. Ripple counter increases but that of synchronous counter remains the same
  - B. Both ripple and synchronous counters increase
  - C. Both ripple and synchronous counters remain the same
  - D. Ripple counter remains the same but that of synchronous counter increases

- B 8. The shift register shown in the figure below is initially loaded with the bit pattern 1010. Subsequently, the shift register is clocked and with each clock pulse the pattern gets shifted by a one-bit position to the right. With each shift, the bit at the serial input is pushed to the leftmost position (MSB). After how many clock pulses will the content of the shift register become 1010 again?

A. 3  
B. 7  
C. 15  
D. 11

 

- D 9. Types of ROM memories are \_\_\_\_\_.


A. EPROM                      B. PROM                      C. EEPROM                      D. All of these

- A 10. The \_\_\_\_\_ is programmable logic device with a fixed OR array and a programmable AND array.

A. PAL                      B. PROM                      C. PLA                      D. None of the above

## Part II: Fill in the blanks space

 
1. The decimal equivalent of the binary 0.1011 is  $(0.6875)_{10} = (11/16)_{10}$
2. In the given figure,  $A = B = 1$  and  $C = D = 0$ . Then  $Y =$  0.




3. The number of product terms in the minimized sum of product expression obtained through the following K-map, where d, don't care is 2 output  $F =$   $\bar{B}\bar{D} + ACD$ .

	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$	
$\bar{A}\bar{B}$	1	0	0	1	
$\bar{A}B$	0	d	0	0	
$AB$	0	0	d	1	$\rightarrow ACD$
$A\bar{B}$	1	0	0	1	

 4. The logic realized by the circuit shown in figure, the output F=



 5. In the given figure shows a 4-bit serial in parallel out right shift register. The initial contents as shown are 0110. After 3 clock pulses the contents will be 1010.



# Q1. BCD to Gray Code Converter Truth table

Decimal	<del>B<sub>3</sub></del> B <sub>3</sub> B <sub>2</sub> B <sub>1</sub> B <sub>0</sub>	G <sub>3</sub>	G <sub>2</sub>	G <sub>1</sub>	G <sub>0</sub>
0	0 0 0 0	0	0	0	0
1	0 0 0 1	0	0	0	1
2	0 0 1 0	0	0	1	1
3	0 0 1 1	0	0	1	0
4	0 1 0 0	0	1	1	0
5	0 1 0 1	0	1	1	1
6	0 1 1 0	0	1	0	1
7	0 1 1 1	0	1	0	0
8	1 0 0 0	1	1	0	0
9	1 0 0 1	1	1	0	1

K-map for G<sub>3</sub>

B <sub>3</sub> B <sub>2</sub> \ B <sub>1</sub> B <sub>0</sub>	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	X	X	X	X
10	1	1	X	X

$$G_3 = B_3$$

For G<sub>2</sub>

B <sub>3</sub> B <sub>2</sub> \ B <sub>1</sub> B <sub>0</sub>	00	01	11	10
00	0	0	0	0
01	1	1	1	1
11	X	X	X	X
10	1	1	X	X

$$G_2 = B_2 + B_3$$

for G<sub>1</sub>

B <sub>3</sub> B <sub>2</sub> \ B <sub>1</sub> B <sub>0</sub>	00	01	11	10
00	0	0	1	1
01	1	1	0	0
11	X	X	X	X
10	0	0	X	X


$$G_1 = B_2 \bar{B}_1 + B_3 \bar{B}_2 B_1 = B_1 \oplus B_2$$

K-map for G<sub>0</sub>

B <sub>3</sub> B <sub>2</sub> \ B <sub>1</sub> B <sub>0</sub>	00	01	11	10
00		1		1
01		1		1
11	X	X	X	X
10		1	X	X

$$G_0 = \bar{B}_1 B_0 + B_1 \bar{B}_0 = B_1 \oplus B_0$$

Circuit Implementation

 




# Solution 2

①

①

Decimal no	Select Lines A B C D	Output Y
0	0 0 0 0	1
1	0 0 0 1	1
2	0 0 1 0	0
3	0 0 1 1	1
4	0 1 0 0	1
5	0 1 0 1	0
6	0 1 1 0	0
7	0 1 1 1	0
8	1 0 0 0	1
9	1 0 0 1	1
10	1 0 1 0	0
11	1 0 1 1	0
12	1 1 0 0	0
13	1 1 0 1	1
14	1 1 1 0	0
15	1 1 1 1	1

 
② Assume a,b,c as select line and D as data line



③ Implement in Table

	D	D	
$D_0$	0	1	1
$D_1$	2	3	D
$D_2$	4	5	$\bar{D}$
$D_3$	6	7	0
$D_4$	8	9	1
$D_5$	10	11	0
$D_6$	12	13	0
$D_7$	14	15	D

 4 Implementation of Circuit using 8:1 MUX




$D_0 = A_1 = 1$   
 $D_1 = D_6 = D_7 = D$   
 $D_2 = \bar{D}$   
 $D_3 = D_5 = 0$

1.5

Design the 3-bit up/down counter using JK FF  
 $M=0$ , Count down,  $M=1$ , Count up

Step 1 State diagram

 

Step 2 Excitation Table

Output $Q_2, Q_1, Q_0$	FF Input		
	J	K	
0 0 0	0	0	X
0 0 1	0	1	X
0 1 0	1	0	X
0 1 1	1	1	X

Step 3 & 4 State diagram and next state Table.

Control	Present state			next state			FF Input					
	$Q_2$	$Q_1$	$Q_0$	$Q_2$	$Q_1$	$Q_0$	$J_2$	$K_2$	$J_1$	$K_1$	$J_0$	$K_0$
0	0	0	0	1	1	1	1	X	1	X	1	X
0	0	0	1	0	0	0	0	X	0	X	1	X
0	0	1	0	0	0	1	0	X	X	0	1	X
0	0	1	1	0	1	0	0	X	X	0	1	X
0	1	0	0	1	0	0	0	X	1	X	1	X
0	1	0	1	1	0	1	0	X	X	1	1	X
0	1	1	0	1	1	0	0	X	0	1	1	X
0	1	1	1	0	1	1	0	X	0	1	1	X
1	0	0	0	0	0	0	0	0	0	0	0	0
1	0	0	1	0	0	1	0	0	0	0	0	0
1	0	1	0	0	0	0	0	0	0	0	0	0
1	0	1	1	0	0	1	0	0	0	0	0	0
1	1	0	0	0	0	0	0	0	0	0	0	0
1	1	0	1	0	0	1	0	0	0	0	0	0
1	1	1	0	0	1	0	0	0	0	0	0	0
1	1	1	1	0	1	1	0	0	0	0	0	0

following pairs of different effective bad resistance to

## Step 5 k-maps



$$I_0 = k_0 = H_0(AH \cdot U)$$

### Step-6 logic Expression


$$J_1 = K_1 = M_{Q_0} + M_{\bar{Q}_0} = \overline{M \oplus Q_0}$$

$$J_0 = k_0 = 1 \text{ (H)}$$

## Step-7 - Counter Implementation



$$G_{11} = M_{10}, G_{12} = M_{11}$$

 



Present State	Input	Next State	Output	T-Map			S-E FF			
$Q_A Q_B Q_C$	$X$	$Q_A^+ Q_B^+ Q_C^+$	$Y$	$T_A$	$T_B$	$T_C$	$S_A R_A$	$S_B R_B$	$S_C R_C$	
0 0 0	0	0 1 1	0	0	1	1	0	X	1	0 1 0
0 0 0	1	1 0 0	1	1	0	0	1	0	X	0 X
0 0 1	0	0 0 1	0	0	0	0	0	X	0 X	X 0
0 0 1	1	1 0 1	1	1	0	1	1	0	X	0 1
0 1 0	0	0 1 0	0	0	1	0	0	X	X 0	0 X
0 1 0	1	0 0 0	1	0	0	1	0	X	0 1	X 0
0 1 1	0	0 1 1	0	0	1	0	0	X	0 1	X 0
0 1 1	1	1 1 1	1	1	0	1	1	0	X	0 1
1 0 0	0	0 1 0	0	0	1	0	0	X	X 0	0 1
1 0 0	1	1 1 0	1	1	0	1	1	0	X	0 X
1 0 1	0	0 1 1	0	0	1	0	0	X	0 1	X 0
1 0 1	1	1 1 1	1	1	0	1	1	0	X	0 1

K-map for T

$Q_A Q_B$	00	01	11	10
0	0	1	1	0
1	0	0	0	0

$Q_B Q_C$	00	01	11	10
0	1	0	0	0
1	0	1	1	1

$Q_A Q_C$	00	01	11	10
0	1	0	1	0
1	0	0	1	0

$T_A = Q_A + \bar{Q}_B X$

$T_B = Q_A + \bar{Q}_B \bar{Q}_C \bar{X} + Q_B Q_C X + Q_B Q_C \bar{X}$   
 $= Q_A + \bar{Q}_B \bar{Q}_C \bar{X} + Q_B (Q_C X + \bar{Q}_C \bar{X})$

$T_C = Q_A X + Q_C X + \bar{Q}_A \bar{Q}_B \bar{Q}_C \bar{X}$   
 $= X(Q_A + Q_C) + \bar{Q}_A \bar{Q}_B \bar{Q}_C \bar{X}$

K-map for S

$Q_A Q_B$	00	01	11	10
0	0	1	1	0
1	0	0	0	0

$S_A = \bar{Q}_A \bar{Q}_B X$

$S_B = Q_A + \bar{Q}_C \bar{X}$

$S_C = Q_A X + \bar{Q}_A \bar{Q}_B \bar{X}$

K-map for R

$Q_A Q_B$	00	01	11	10
0	0	1	1	0
1	0	0	0	0

$R_A = Q_A$

K-map for R<sub>B</sub>

$Q_B Q_C$	00	01	11	10
0	1	0	0	0
1	0	1	1	1

$R_B = \bar{Q}_B \bar{Q}_C X + Q_C \bar{X}$

K-map for R<sub>C</sub>

$Q_A Q_C$	00	01	11	10
0	1	0	1	0
1	0	0	1	0

$R_C = Q_C X$

K-map for O/P Y

$Q_A Q_B$	00	01	11	10
0	0	1	1	0
1	0	0	0	0

$Y = \bar{Q}_A X$

the following pairs of different effective and desirable



Q5 → Design a 4-bit Johnson Counter using D-FF

	$Q_A$	$Q_B$	$Q_C$	$Q_D$	$Q_A'$	$Q_B'$	$Q_C'$	$Q_D'$	$D_A$	$D_B$	$D_C$	$D_D$
Initial	0	0	0	0	1	0	0	0	1	0	0	0
1	1	0	0	0	1	1	0	0	1	1	0	0
2	1	1	0	0	1	1	1	0	1	1	1	0
3	1	1	1	0	1	1	1	1	0	1	1	1
4	1	1	1	1	0	1	1	1	0	0	1	1
5	0	1	1	1	0	0	1	1	0	0	0	1
6	0	0	1	1	0	0	0	1	0	0	0	0
7	0	0	0	1	0	0	0	0	0	0	0	0
8												

K-map  $D_A$

$Q_C Q_D$	00	01	11	10
$Q_A Q_B$				
00	1	0	0	X
01	X	X	0	X
11	1	X	0	1
10	1	X	X	X

$$D_A = \bar{Q}_D$$

$D_B$

$Q_C Q_D$	00	01	11	10
$Q_A Q_B$				
00	0	0	0	X
01	X	X	0	X
11	1	X	1	1
10	1	X	X	X

$$D_B = Q_A$$

$D_C$

$Q_C Q_D$	00	01	11	10
$Q_A Q_B$				
00	0	0	0	X
01	X	X	1	X
11	1	X	1	1
10	0	X	X	X

$$D_C = Q_B$$

$D_D$

$Q_C Q_D$	00	01	11	10
$Q_A Q_B$				
00	0	0	1	X
01	X	X	1	X
11	0	X	1	1
10	0	X	X	X

$$D_D = Q_C$$

